

# **M66-DS** Reference Design

**GSM/GPRS Module Series**

Rev. A

Date: 2016-03-14



**Our aim is to provide customers with timely and comprehensive service. For any assistance, please contact our company headquarters:**

**Quectel Wireless Solutions Co., Ltd.**

Office 501, Building 13, No.99, Tianzhou Road, Shanghai, China, 200233

Tel: +86 21 5108 6236

Mail: [info@quectel.com](mailto:info@quectel.com)

**Or our local office, for more information, please visit:**

<http://www.quectel.com/support/salesupport.aspx>

**For technical support, to report documentation errors, please visit:**

<http://www.quectel.com/support/techsupport.aspx>

Or Email: [Support@quectel.com](mailto:Support@quectel.com)

**GENERAL NOTES**

QUECTEL OFFERS THIS INFORMATION AS A SERVICE TO ITS CUSTOMERS. THE INFORMATION PROVIDED IS BASED UPON CUSTOMERS' REQUIREMENTS. QUECTEL MAKES EVERY EFFORT TO ENSURE THE QUALITY OF THE INFORMATION IT MAKES AVAILABLE. QUECTEL DOES NOT MAKE ANY WARRANTY AS TO THE INFORMATION CONTAINED HEREIN, AND DOES NOT ACCEPT ANY LIABILITY FOR ANY INJURY, LOSS OR DAMAGE OF ANY KIND INCURRED BY USE OF OR RELIANCE UPON THE INFORMATION. THE INFORMATION SUPPLIED HEREIN IS SUBJECT TO CHANGE WITHOUT PRIOR NOTICE.

**COPYRIGHT**

THIS INFORMATION CONTAINED HERE IS PROPRIETARY TECHNICAL INFORMATION OF QUECTEL CO., LTD. TRANSMITTABLE, REPRODUCTION, DISSEMINATION AND EDITING OF THIS DOCUMENT AS WELL AS UTILIZATION OF THIS CONTENTS ARE FORBIDDEN WITHOUT PERMISSION. OFFENDERS WILL BE HELD LIABLE FOR PAYMENT OF DAMAGES. ALL RIGHTS ARE RESERVED IN THE EVENT OF A PATENT GRANT OR REGISTRATION OF A UTILITY MODEL OR DESIGN.

***Copyright © Quectel Wireless Solutions Co., Ltd. 2016. All rights reserved.***

## History

Revision	Date	Author	Description
A	2016-03-14	Felix YIN	Initial

Quectel  
Confidential

## Contents

<b>1</b>	<b>Reference Schematic.....</b>	<b>4</b>
1.1.	Introduction .....	4
1.2.	Schematics .....	4

Quectel  
Confidential

# 1 Reference Schematic

## 1.1. Introduction

This document is a reference design for M66-DS module. The schematics included in this document are preliminary and are subject to change without notice.


## 1.2. Schematics

Quectel  
Confidential

# Module Design

Charge golden capacitor or battery when VBAT is applied.


If unused, keep VRTC open.

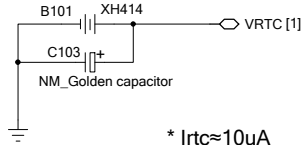

\* Irtc≈10uA

\* As only powering the VRTC pin to keep the RTC will lead an error for about 5 minutes a day, it is recommended to power VBAT and VRTC pin at the same time when RTC function is needed. For more details, please refer to M66-DS HD.

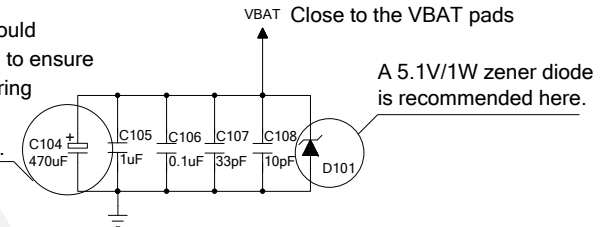
Capacitance of C104 should be chosen by debugging to ensure the max voltage drop during the burst transmission does not exceed 400mV.




A 5.1V/1W zener diode is recommended here.

- VBAT ranges from 3.3V to 4.6V.
- Module drains the maximum current around 1.6A in burst time (577us).
- The width of VBAT trace is recommended to be more than 2mm.
- Capacitance is arranged in ascending order, with the smallest one closing to the VBAT pad, and all capacitance as close to the VBAT pad as possible.

## Reference Circuit of ADC

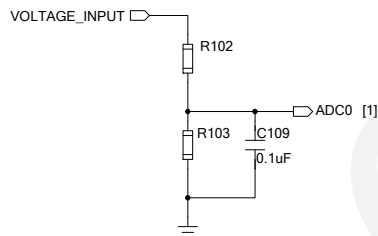

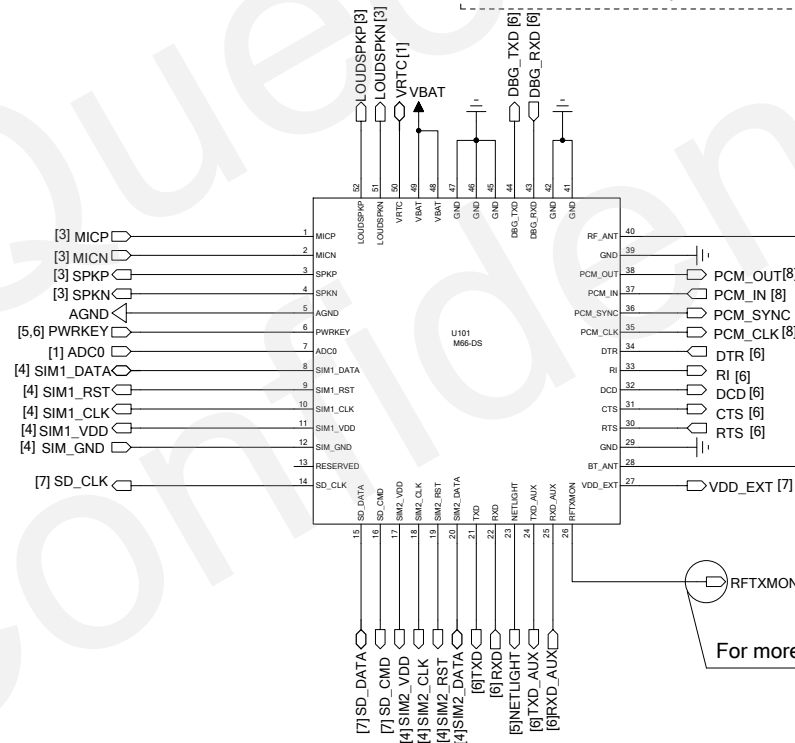- \* The voltage range of ADC input channel is from 0 to 2.8V.
- \* Please select a high-precision divider resistance.



For RF layout, please refer to RF\_Layout\_Application\_Note. A Pi match circuit is recommended to be added.

For more details about RFTXMON, please refer to M66-DS HD.

## Quectel Wireless Solutions

DRAWN BY Felix YIN	PROJECT M66-DS	TITLE Reference Design
CHECKED BY Tony GAO	SIZE A2	VER A
SHEET	1 OF 8	DATE 2016/3/14


# Power Supply

## NOTE

The voltage converter should provide a minimum current of 2.0A.

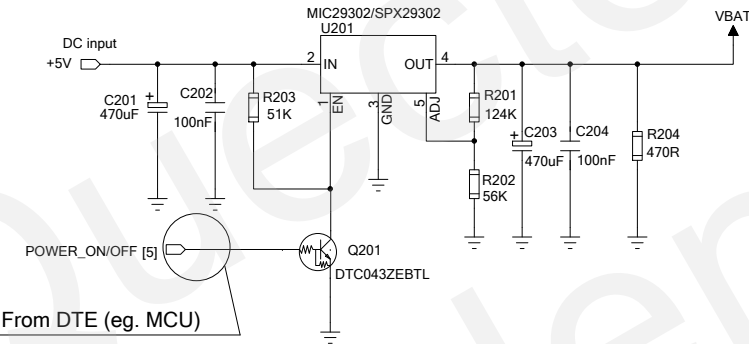
## LDO Application

It is used when the DC input voltage is below 7V.



## DC-DC Application

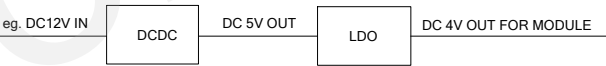1. It can be used when the input voltage is above 7V in vehicle application.
2. Use DCDC to convert high input voltage to 5V and LDO will generate 4V typical voltage for the module.



### Quectel Wireless Solutions


DRAWN BY Felix YIN	PROJECT M66-DS	TITLE Reference Design
CHECKED BY Tony GAO	SIZE A2	VER A
SHEET	2 OF 8	DATE 2016/3/14

# Audio Design


## NOTES

1. AGND is recommended to be routed separately.
2. 10pF & 33pF capacitors are used for filtering TDD noise.
3. AIN has bias voltage of microphone.
4. AOUT1 is capable of driving 32ohm load.
5. AOUT2 is capable of driving 8ohm load and Earphone.
6. These components are used to enhance the ESD performance of MIC lines, and thus it is strongly recommended to reserve them.


## Handsets Application of AIN/AOUT1

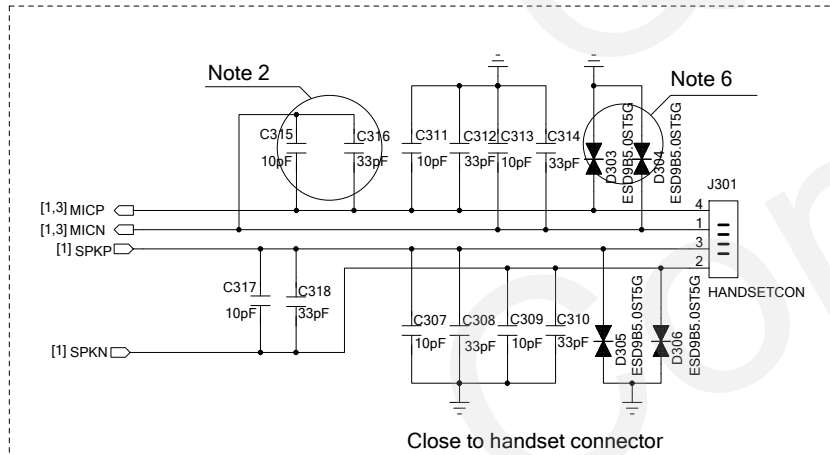

## Hands-free Application of AIN/AOUT2

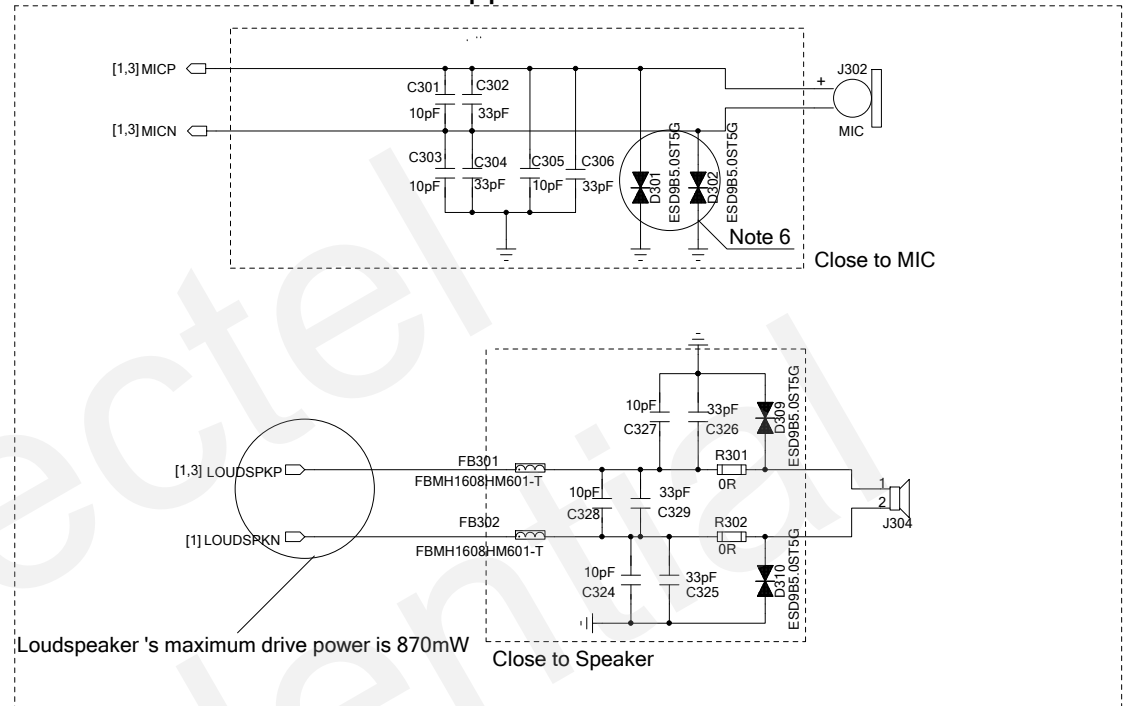

## Earphone Application of AIN/AOUT2

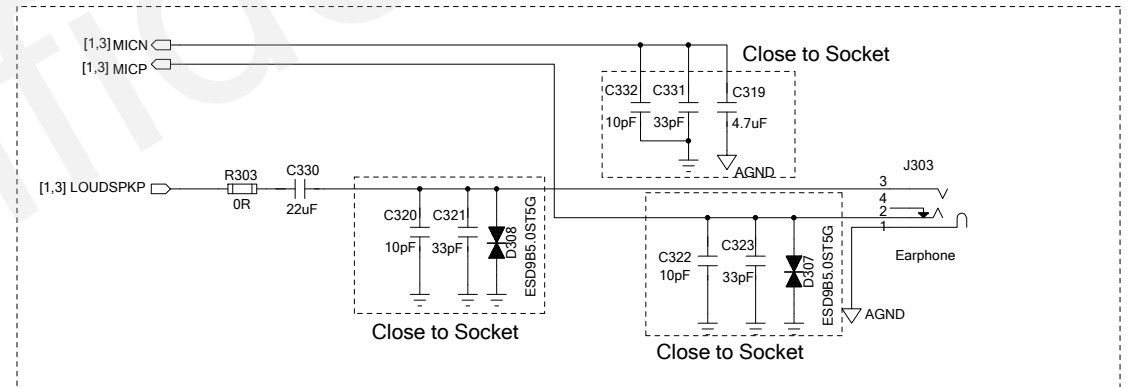


## Quectel Wireless Solutions

DRAWN BY Felix YIN	PROJECT M66-DS	TITLE Reference Design
CHECKED BY Tony GAO	SIZE A2	VER A
SHEET	3 OF 8	DATE 2016/3/14



# SIM Card

## SIM Card Interface

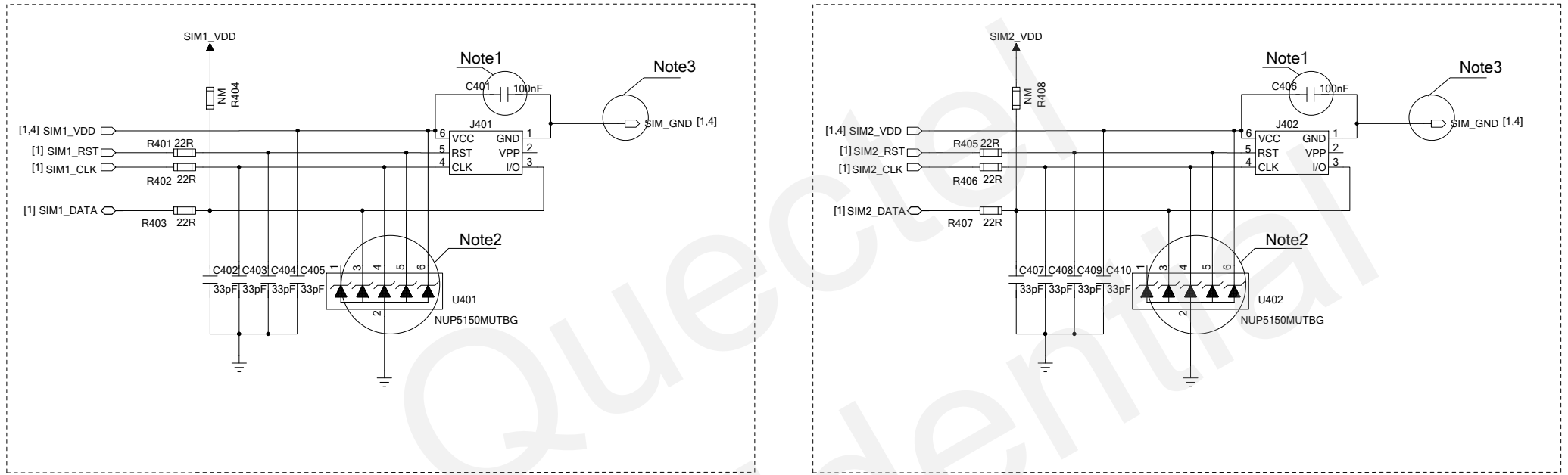

### NOTES


1. The value of C401 and C406 should be less than 1uF.
2. U401 and U402 is used for protecting SIM card against ESD, and the junction capacitance should be less than 50pF. It should be placed nearby SIM card holder.
3. For M66-DS module, ground of SIM card is recommended to be routed to the Pin 12 ("SIM\_GND") of the module separately.

### Quectel Wireless Solutions


DRAWN BY Felix YIN	PROJECT M66-DS	TITLE Reference Design
CHECKED BY Tony GAO	SIZE A2	VER A
SHEET	4 OF 8	DATE 2016/3/14

Driver


Turn On/Off

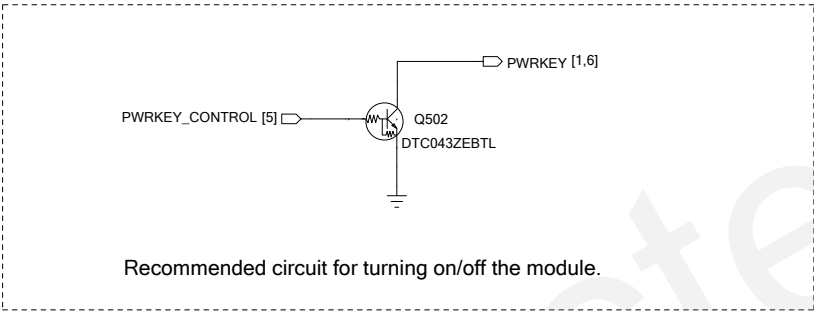

LED Indication

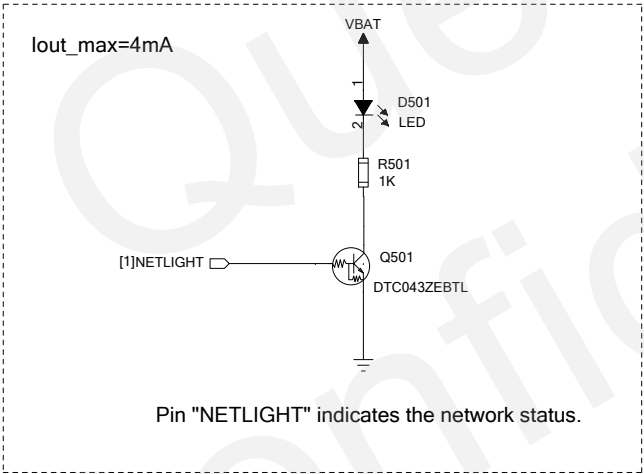

MCU GPIO

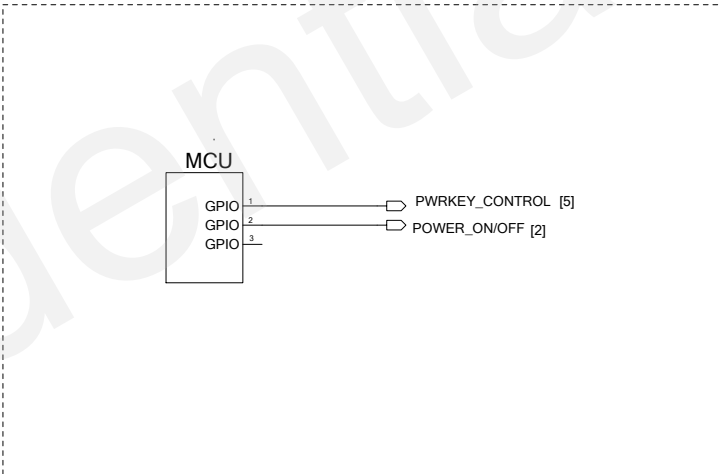

Quectel Wireless Solutions

DRAWN BY Felix YIN	PROJECT M66-DS	TITLE Reference Design
CHECKED BY Tony GAO	SIZE A2	VER A
SHEET	5 OF 8	DATE 2016/3/14

# Serial Interface

Electric characteristics of the module's input and output port:

$VOH_{min}=0.85*VDD\_EXT$

$VOL_{max}=0.15*VDD\_EXT$


$VIL_{max}=0.25*VDD\_EXT$

$VIH_{min}=0.75*VDD\_EXT$

$VIH_{max}=VDD\_EXT+0.2V$


$VDD\_EXT=2.8V$  (typical value)
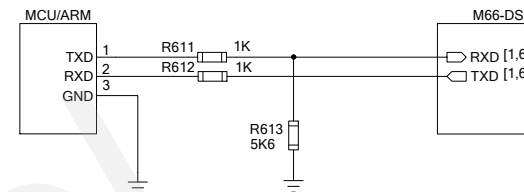
## Connection of Three-line UART Port for 3.3V System



\* Please pay attention to the level match of UART in product application.

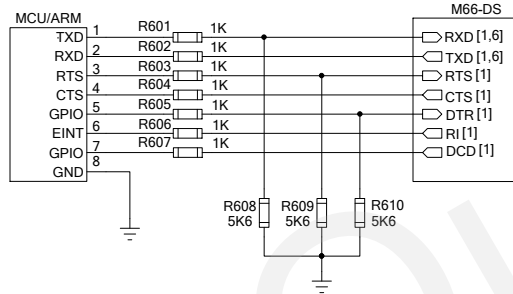
## Connection of All Functional UART Port for 3.3V System



### NOTES


1. CTS&RTS will be used for HW flow control when mass data has been sent.
2. When AT+QSCCLK=1 is set on the module, customer's application can control the module to enter into or exit from the sleep mode through the pin DTR. When DTR is set to high level, and there is no on-air or hardware interrupt, such as GPIO interrupt or data on serial port, the module will enter into sleep mode automatically.
3. RI will output an indication signal when activity such as voice call or SMS is coming.
4. DCD is mainly applied in modem communication (PPP). The active status represents the communication link has been set up.
5. Please pay attention to the level match of UART in product application.
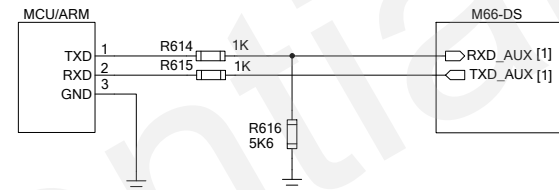
## Connection of Three-line AUX\_UART Port for 3.3V System




\* Please pay attention to the level match of UART in product application.

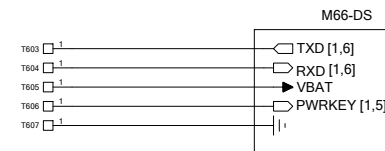It is recommended to reserve the points for upgrading the firmware.



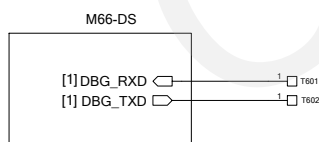\* Please pay attention to the level match of UART in product application.




It is recommended to reserve the points for debug port.

### Quectel Wireless Solutions

DRAWN BY Felix YIN	PROJECT M66-DS	TITLE Reference Design
CHECKED BY Tony GAO	SIZE A2	VER A
SHEET	6 OF 8	DATE 2016/3/14

## SD Card Interface

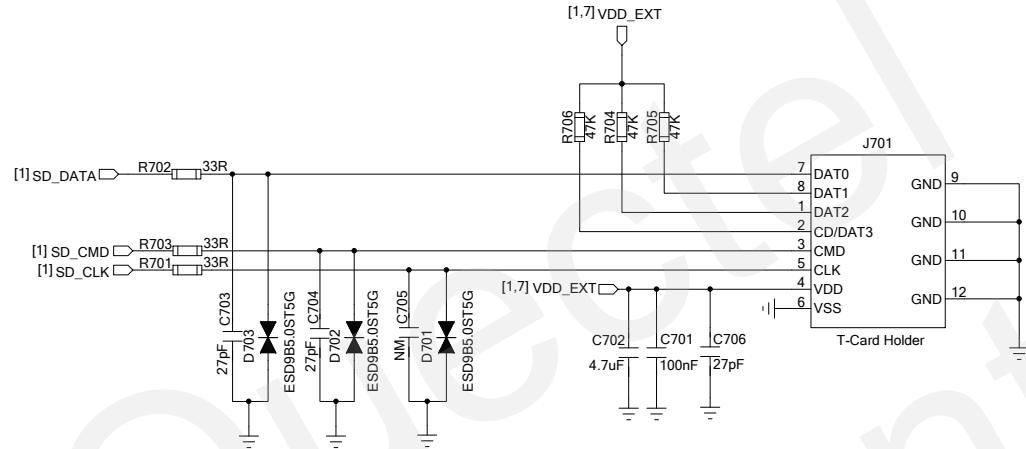

### Design Notes:

1. SPI mode memory card is not supported.
2. Hot plug is not supported.
3. It is recommended to add transient voltage suppressor with less than 15pF junction capacitance for ESD protection.


### Layout Notes:

1. Keep all SD card lines far away from the power and RF trace.
2. Route all SD card signals as short as possible. Ensure the length of every trace does not exceed 100mm.
3. The SD\_CLK, SD\_DATA and SD\_CMD trace should be routed together. Keep trace difference of SD card signals less than 10mm.
4. Reserve external pull-up resistor for other data lines except the DATA0.
5. The SD\_CLK and SD\_DATA signals must be protected by ground in order to improve EMI.

### Quectel Wireless Solutions

DRAWN BY Felix YIN	PROJECT M66-DS	TITLE Reference Design
CHECKED BY Tony GAO	SIZE A2	VER A
SHEET	7 OF 8	DATE 2016/3/14

# PCM Design

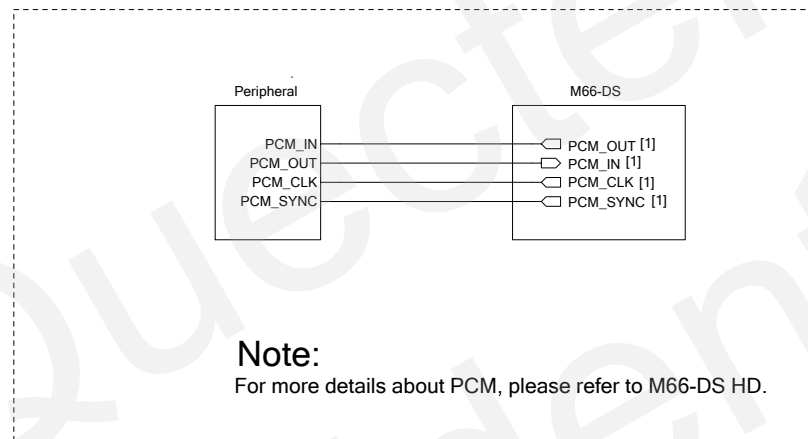

## Qectel Wireless Solutions

DRAWN BY Felix YIN	PROJECT M66-DS	TITLE Reference Design
CHECKED BY Tony GAO	SIZE A2	VER A
SHEET	8 OF 8	DATE 2016/3/14